

**Question 2**

What is the value of  $i_b$  in Figure 2? Find the value of resistance  $R$  that gives rise to a magnitude of 6V being measured by the voltmeter in the same figure.

(10 marks)



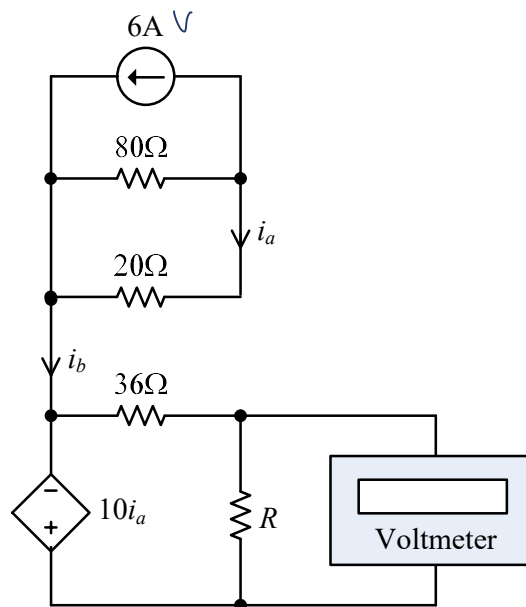


Figure 2

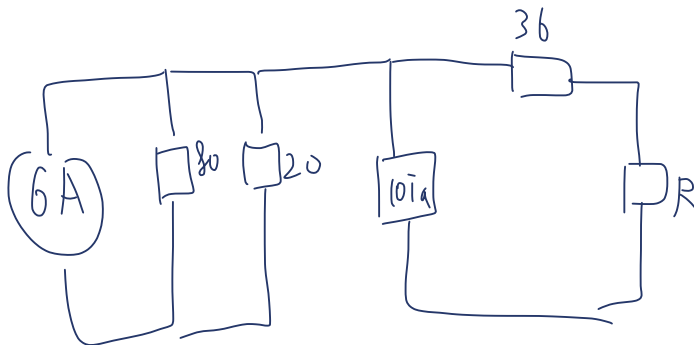

$$\text{For } i_a, i_a = 6A \cdot \frac{80}{80+20} = -4.8A$$
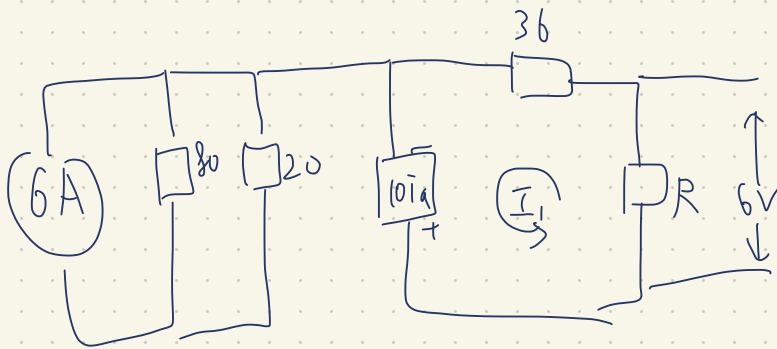
$$\therefore \text{voltage source is } 10i_a = -48V$$



By KVL

$$6V - 36i_1 + (-48)I_1 = 0$$

$$\therefore i_1 = 0.1071428571$$

$$\text{where } i_b = i_1 = 0.107143 \text{ A}$$

$$\text{For } I_1 \cdot R = 6$$

$$R = 84 \Omega$$

$\therefore$  Required Resistance is  $84 \Omega$