

**Question 3**

For the circuit shown in Figure 3, prove that if  $\Delta R \ll R$  ( $\ll$  means much smaller than), output voltage  $v_o$  can be approximated as (ideal op-amp can be assumed):

$$v_o \approx \frac{R_f}{R^2} \left( \frac{R + R_f}{R + 2R_f} \right) (-\Delta R) v_{in}$$

(30 marks)

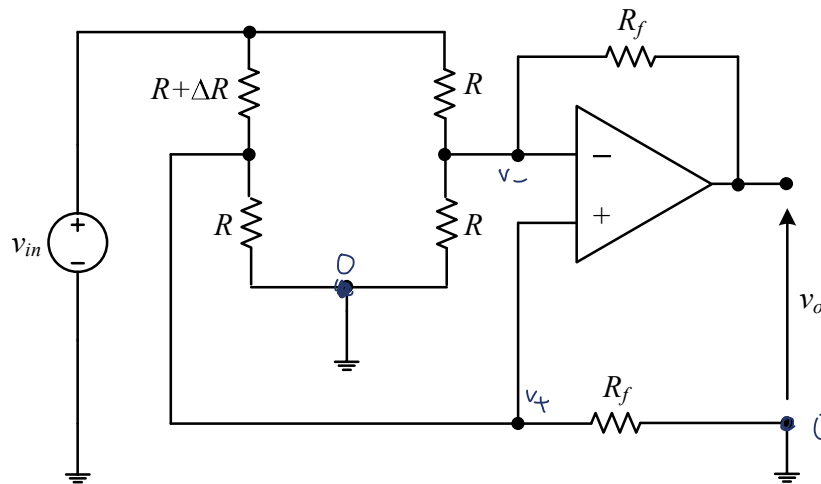


Figure 3

For  $V_-$  and  $V_+$ , ideal amplifier  $V_- = V_+$

At node  $V_+$ , by KCL,

$$\frac{V_+ - v_{in}}{R + \Delta R} + \frac{V_+ - 0}{R_f} + \frac{V_+ - 0}{R} = 0$$

$$V_+ = \frac{v_{in}}{R + \Delta R} \left( \frac{1}{R + \Delta R} + \frac{1}{R_f} + \frac{1}{R} \right)^{-1}$$

$$= \frac{v_{in}}{R + \Delta R} \left( \frac{R_f R + (R + \Delta R) R + (R + \Delta R) R_f}{(R + \Delta R) (R_f) (R)} \right)^{-1}$$

$$= \frac{v_{in} (R + \Delta R) (R_f) (R)}{(R + \Delta R) (R_f R + (R + \Delta R) R + (R + \Delta R) R_f)}$$

$$= \frac{v_{in} (R_f) (R)}{R_f R + (R + \Delta R) R + (R + \Delta R) R_f}$$

At node  $V_-$ ,

$$\frac{V_- - V_{in}}{R} + \frac{V_- - 0}{R} + \frac{V_- - V_{out}}{R_f} = 0$$

$$\frac{1}{R} (2V_- - V_{in}) + \frac{V_-}{R_f} - \frac{V_{out}}{R_f} = 0$$

$$V_- \left( \frac{2}{R} + \frac{1}{R_f} \right) = \frac{V_{out}}{R_f} + \frac{V_{in}}{R}$$

$$V_- (2R_f + R) = V_{out} R + V_{in} R_f$$

$$V_{out} = \frac{V_- (2R_f + R)}{R} - \frac{V_{in} R_f}{R}$$

$$V_- = \frac{V_{out} R + V_{in} R_f}{2R_f + R}$$

$$\therefore V_+ = V_- = \frac{V_{in} (R_f) (R)}{(R_f R + (R + \Delta R) R + (R + \Delta R) R_f)}$$

$$\therefore V_{out} = \frac{V_{in} (R_f) (R)}{(R_f R + (R + \Delta R) R + (R + \Delta R) R_f)} (2R_f + R) - \frac{V_{in} R_f}{R}$$

$$= (V_{in}) \left( \frac{2R_f^2 + R_f R}{(R_f R + (R + \Delta R) R + (R + \Delta R) R_f)} - \frac{R_f}{R} \right)$$

$$= (V_{in}) \frac{2R_f^2 R + R_f R^2 - R_f^2 R - R^2 R_f - \Delta R R R_f - R_f^2 R - \Delta R R_f^2}{R (R_f R + (R + \Delta R) R + (R + \Delta R) R_f)}$$

$$= (V_{in}) \left( \frac{-\Delta R R_f R - \Delta R R_f^2}{R (R_f R + (R + \Delta R) R + (R + \Delta R) R_f)} \right)$$

$$v_o \approx \frac{R_f}{R^2} \left( \frac{R + R_f}{R + 2R_f} \right) (-\Delta R) v_{in}$$

$$= (V_{in}) (-\Delta R) \frac{R_f (R + R_f)}{R (R_f R + (R + \Delta R) R + (R + \Delta R) R_f)}$$

$$\therefore \text{if } \Delta R \ll R, (R + \Delta R) = R$$

$$= (V_{in}) (-\Delta R) \frac{R_f (R + R_f)}{R (R_f R + (R) R + (R) R_f)}$$

$$= (V_{in}) (-\Delta R) \frac{R_f}{R^2} \left( \frac{R + R_f}{R_f + R + R_f} \right)$$

$$= \frac{R_f}{R^2} \left( \frac{R + R_f}{R + 2R_f} \right) (-\Delta R) (V_{in})$$