

香 港 中 文 大 學
The Chinese University of Hong Kong

版權所有 不得翻印
Copyright Reserved

二零二零至二一年度上學期科目考試

Course Examination 1st Term, 2020-21

科目編號及名稱

Course Code & Title : ELEG2202A – Fundamental of Electric Circuits

時間

小時

分鐘

Time allowed :

2

hours

0

minutes

學號

座號

Student I.D. No. :

Seat No. :

Total of **FOUR** questions

Marks for each question are indicated next to it

Answers for all **FOUR** questions must be written on the provided answer book

Question 1

Calculate the power generated by each source for all voltage sources and current sources shown in Figure 1. Prove that principle of conservation of power is indeed true.

(35 marks)

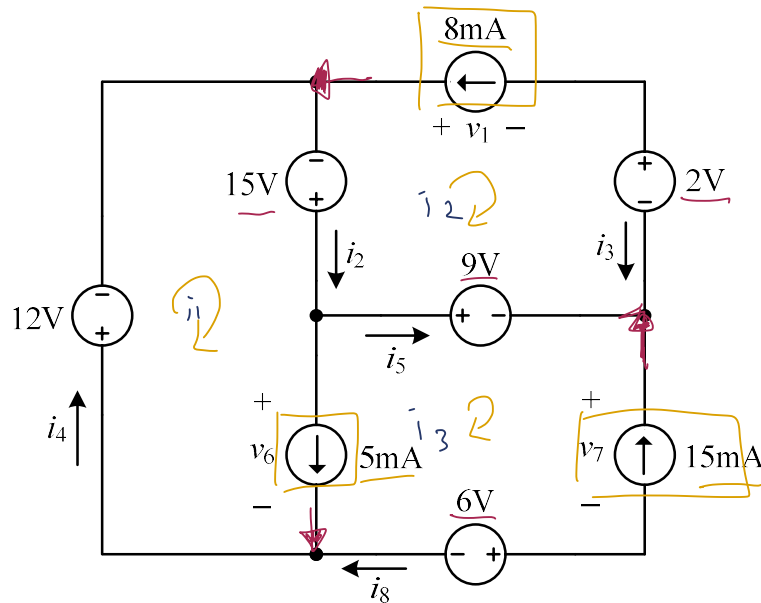


Figure 1

$$\text{For Mesh 1, } 12i_1 - 15(i_1 - i_2) - v_6 = 0$$

$$\text{Mesh 2 } 15(i_2 - i_1) - 9(i_2 - i_3) + 2i_2 + v_1 = 0$$

$$\text{Mesh 3 } 6i_3 + 9(i_3 - i_2) + v_6 + v_7 = 0$$

$$\text{supermesh 1, } 12i_1 + v_1 + 2i_2 + 15i_3 + 6i_5 = 0$$

$$\text{supermesh 2, } 15i_2 + v_1 + 2i_2 + v_7 + 6i_3 + v_6 = 0$$

$$12i_1 - 15(i_1 - i_2) + 9 = 0 \rightarrow (1)$$

$$17i_2 + 6i_3 - 17 = 0 \rightarrow (2)$$

$$\text{By 1, } -3i_1 + 15i_2 = -9$$

$$i_2 = \frac{-9 - 3i_1}{15}$$

$$\text{For } v_6 = 12 - 15 - 6 = -9\text{V}$$

$$\therefore \text{ current source Power} = -9 \cdot 5\text{mA} = -0.045\text{W}$$

$$\text{For } v_1 = -2 + -15 + 9 = -8\text{V}$$

$$\therefore \text{ current source Power} = -8 \cdot 8\text{mA} = -0.064\text{W}$$

$$\text{For } v_7 = -6 + -9 = -15\text{V}$$

$$\text{current source power} = -15 \cdot 15\text{mA} = -0.225\text{W}$$

$$\text{By (2), } 17\hat{i}_2 + 6\hat{i}_3 - 17 = 0$$

$$\hat{i}_3 = \frac{17 - 17\hat{i}_2}{6}$$

Sub it to Mesh 3,

$$6\left(\frac{17 - 17\hat{i}_2}{6}\right) + 9\left(\frac{17 - 17\hat{i}_2}{6}\right)$$

$$-9 \cdot \hat{i}_2 + -9 + -15 = 0$$

$$\therefore \hat{i}_2 = 0.35922$$

$$\therefore \hat{i}_3 = 1.815533981$$

$$\therefore \text{av Power} = 13.11 \text{ W}$$

'