

Ng Chi Hon (155116317)

## Fundamentals of Electric Circuits (ELEG2202A)

### HW1

Q1. (12 pts)

The total charge entering a terminal is given by  $q = 5t \sin(4\pi t)$  mC (millicoulomb). Calculate the current at  $t = 0.5$  s.

Q2. (13 pts) Solve for the current flowing through the  $8\text{-}\Omega$  resistor in Fig.1.

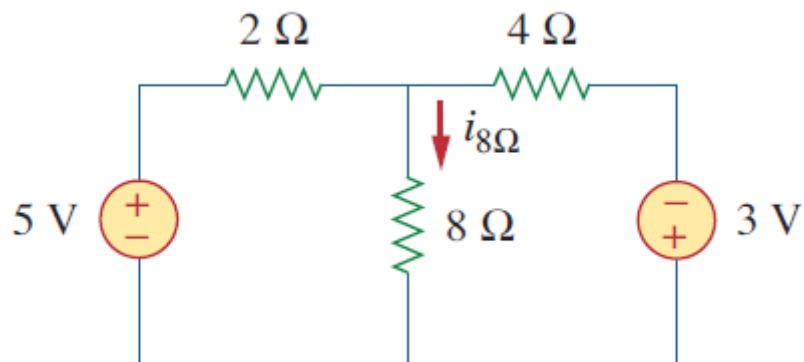


Fig.1

Q3. (20 pts) Find  $R_{ab}$  for the circuit shown in Fig.2.

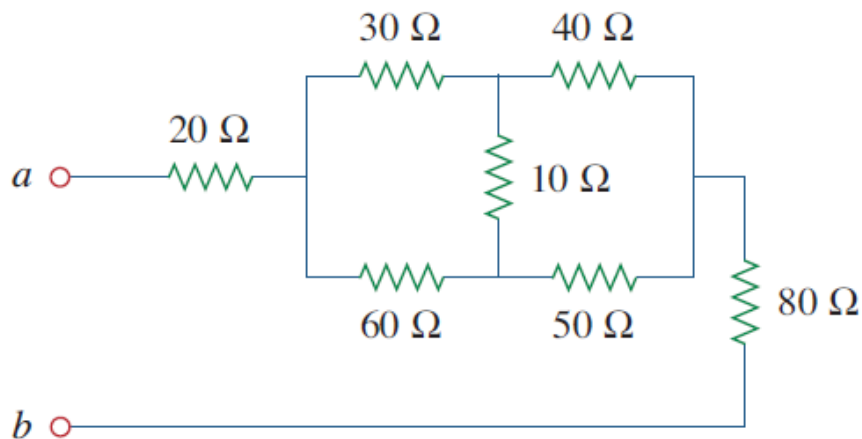


Fig.2

# Fundamentals of Electric Circuits (ELEG2202A)

## HW1

Q1. (12 pts)

The total charge entering a terminal is given by  $q = 5t \sin(4\pi t)$  mC (millicoulomb). Calculate the current at  $t = 0.5$  s.

Q2. (13 pts) Solve for the current flowing through the 8- $\Omega$  resistor in Fig.1.

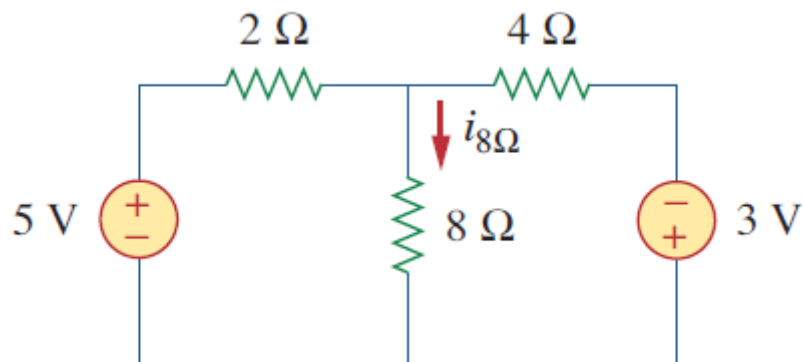


Fig.1

Q3. (20 pts) Find  $R_{ab}$  for the circuit shown in Fig.2.

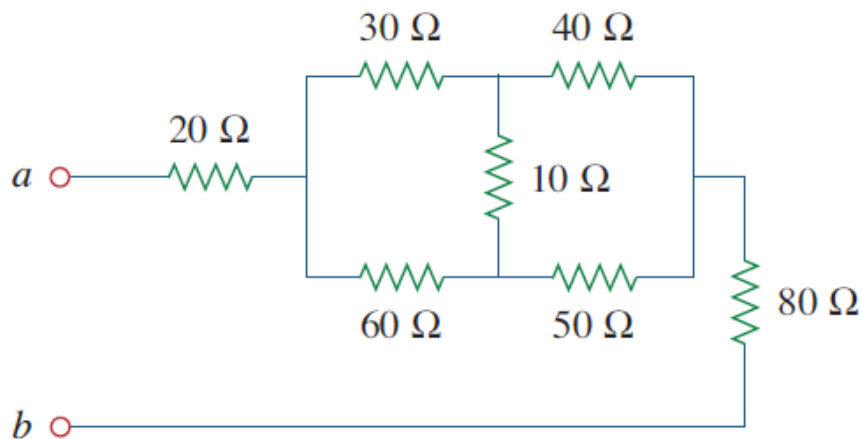


Fig.2

Q4. (25 pts) Find the equivalent resistance  $R_{ab}$  in the circuit of Fig.3.

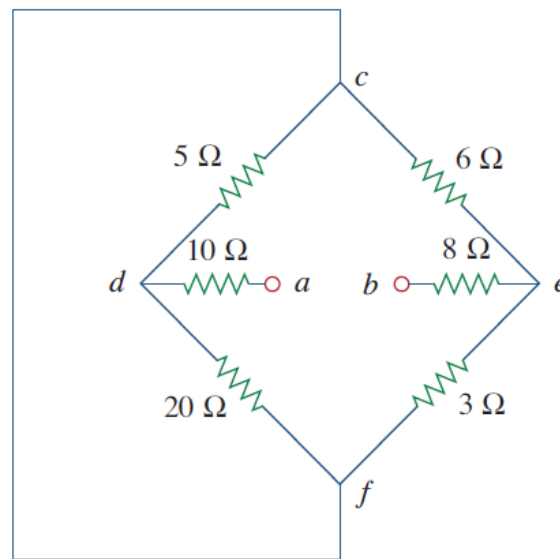


Fig.3

Q5. (30 pts) A network consisting 5 resistors ( $R_1 - R_5$ ) is connected to a voltage source through two terminals a and b (Fig. 4).

1. Calculate the equivalent resistance of  $R_{ab}$ .
2. Calculate the power supplied by  $P_1$ .
3. If define the current direction of  $I$  as entering the positive terminal of  $P_1$ , find the value of  $I$ .


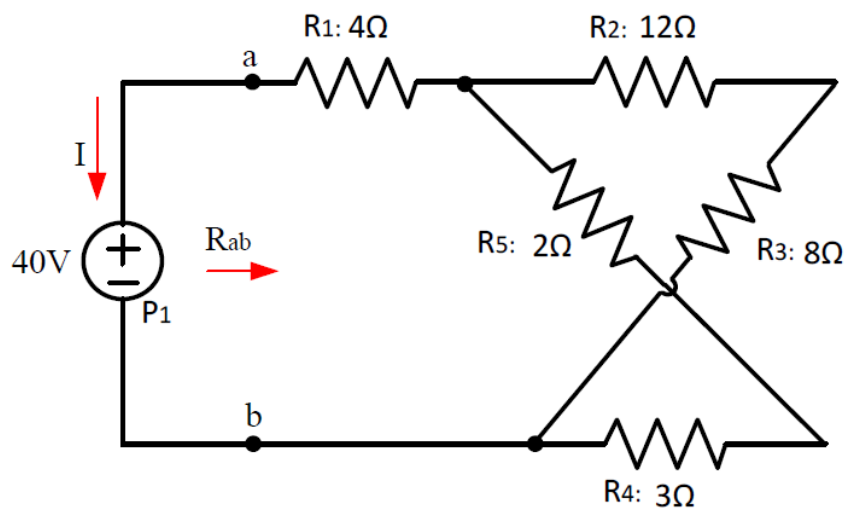


Fig.4

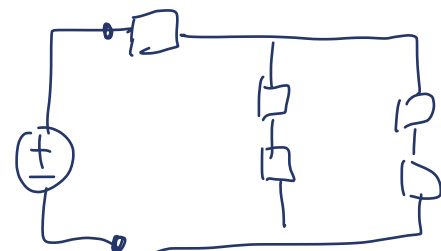


Q1. (12 pts)

The total charge entering a terminal is given by  $q = 5t \sin(4\pi t)$  mC (millicoulomb). Calculate the current at  $t = 0.5$  s.

$$\begin{aligned} I(t) &= \frac{d}{dt}(q(t)) \\ &= \frac{d}{dt}(5t \sin(4\pi t)) \\ &= 5(\sin(4\pi t) + 4\pi t \cos(4\pi t)) \\ \therefore I(0.5) &= 31.7744 \text{ mA} // \end{aligned}$$

Q1. (12 pts)

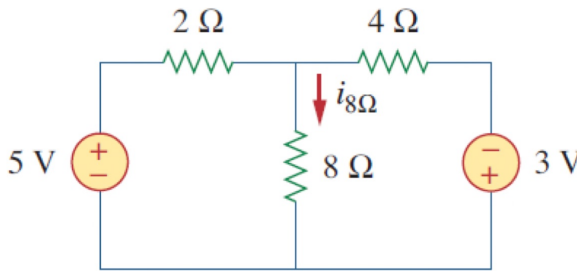Q2. The total charge entering a terminal is given by  $q = 5t \sin(4\pi t)$  mC (millicoulomb). Calculate the current at  $t = 0.5$  s.



250mA

Fig.1


Let  $V_{8\Omega}$  be the voltage at the node between  $1k\Omega$  and  $4k\Omega$

$$\frac{5 - V_{8\Omega}}{2} + \frac{-3 - V_{8\Omega}}{4} = \frac{V_{8\Omega}}{8}$$

$$\begin{aligned} 20 - 4V_{8\Omega} - 6 - 2V_{8\Omega} &= V_{8\Omega} \\ 14 &= 7V_{8\Omega} \\ V_{8\Omega} &= 2 \end{aligned}$$

$$\begin{aligned} \therefore i_{8\Omega} &= \frac{2}{8} \\ &= 250 \text{ mA} // \end{aligned}$$

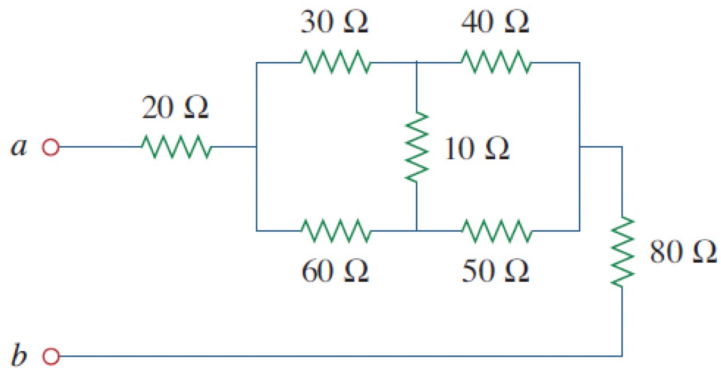Q3. (20 pts) Find  $R_{ab}$  for the circuit shown in Fig.2.



$$R_{a'n} = \frac{40 \cdot 10}{40 + 10 + 50} = 4 \Omega$$

$$R_{b'n} = \frac{10 \cdot 50}{40 + 10 + 50} = 5 \Omega$$

$$R_{c,n} = \frac{40 \cdot 50}{40 + 10 + 50} = 20 \Omega$$

$$\therefore R_{ab} = 20 + 80 + 20 + (30 + 4) \parallel (60 + 5) = 142.32 \Omega //$$

Q4. (25 pts) Find the equivalent resistance  $R_{ab}$  in the circuit of Fig.3.

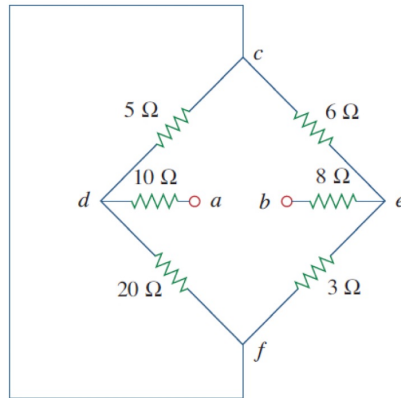


Fig.3


$$Q4) \quad 5 \parallel 20 = \frac{5 \times 20}{25} = 4 \Omega$$

$$6 \parallel 3 = \frac{6 \times 3}{9} = 2 \Omega$$

$$\therefore R_{ab} = 10 + 4 + 2 + 8 = 24 \Omega //$$

Q5. (30 pts) A network consisting 5 resistors ( $R_1 - R_5$ ) is connected to a voltage source through two terminals a and b (Fig. 4).

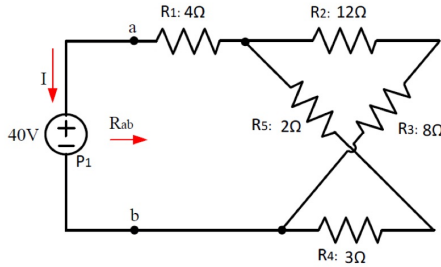1. Calculate the equivalent resistance of  $R_{ab}$ .
2. Calculate the power supplied by  $P_1$ .
3. If define the current direction of  $I$  as entering the positive terminal of  $P_1$ , find the value of  $I$ .



1)  $R_2$  and  $R_3$  in series!  
 $12 + 8 = 20 \Omega$

$R_5$  and  $R_4$  in series  
 $2 + 3 = 5 \Omega$

$$(R_2 + R_3) \parallel (R_5 \text{ and } R_4) = \frac{20 \times 5}{20 + 5} = 4 \Omega$$

$$\therefore R_{ab} = 4 + 4 = 8 \Omega$$

2) Power Supplied =  $\frac{V^2}{R} = \frac{40^2}{8} = 200W$

3) Current =  $\frac{200}{40} = 5A$

$\therefore I$  is  $-5A$  with direction